



---

# ADE LAB SIMULATION

---

Asynchronous Up Counter Simulation



BY:

MOHAMMED YAHYA  
USN: 3PD23CS076

SAINATH PATIL  
USN: 3PD23CS120


SEC: B

# Asynchronous Up Counter

**Aim:** To display 3 bit binary digits from 0 to 7 using asynchronous up counter.

**Theory:** 3 bit asynchronous counter can be made by using sequential circuit of 3 T flip-flop. Then 3-bit binary number can be displayed by 7-segment display using BCD decoder.


## Circuit Diagram:

 

## Truth Table:


Asynchronous counter:

Clock Cycles	<i>Output Bits</i>		
	<i>QC</i>	<i>QB</i>	<i>QA</i>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

 

The binary output from the 3 bit asynchronous counter is given as input to BCD converter and it is displayed by 7 segment display as shown

## BCD to 7 segment decoder:

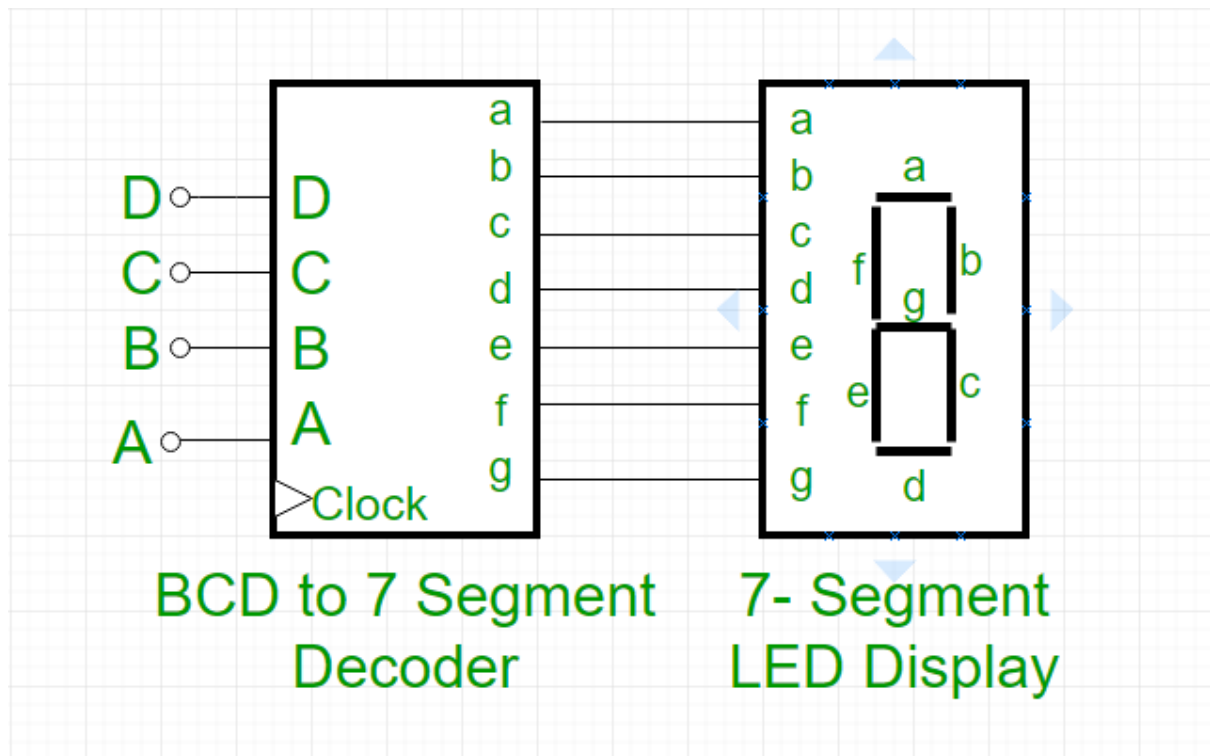

Final output:



